


ITI  
LAB10  
Noise Simulation

## Contents


PART 1: LPF AC Noise Analysis.....	2
Schematic.....	2
Output noise vs frequency with the noise density annotated.....	2
Output noise vs frequency with the bandwidth annotated.....	3
rms output noise.....	3
Hand analysis.....	3
Parametric sweep.....	4
PART 2: LPF Transient Noise Analysis.....	5
PART 3: 5T OTA AC Noise Analysis.....	7
Thermal noise.....	7
Corner frequency.....	8
Rms noise (due to the thermal noise only).....	8
Hand analysis.....	8
PART 4: 5T OTA Transient Noise Analysis.....	10

# PART 1: LPF AC Noise Analysis


## Schematic

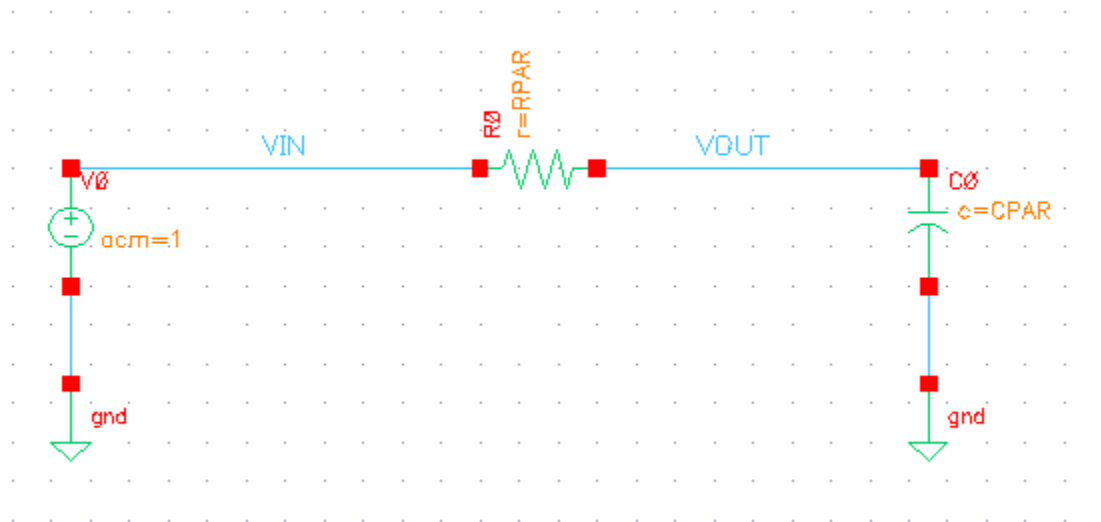
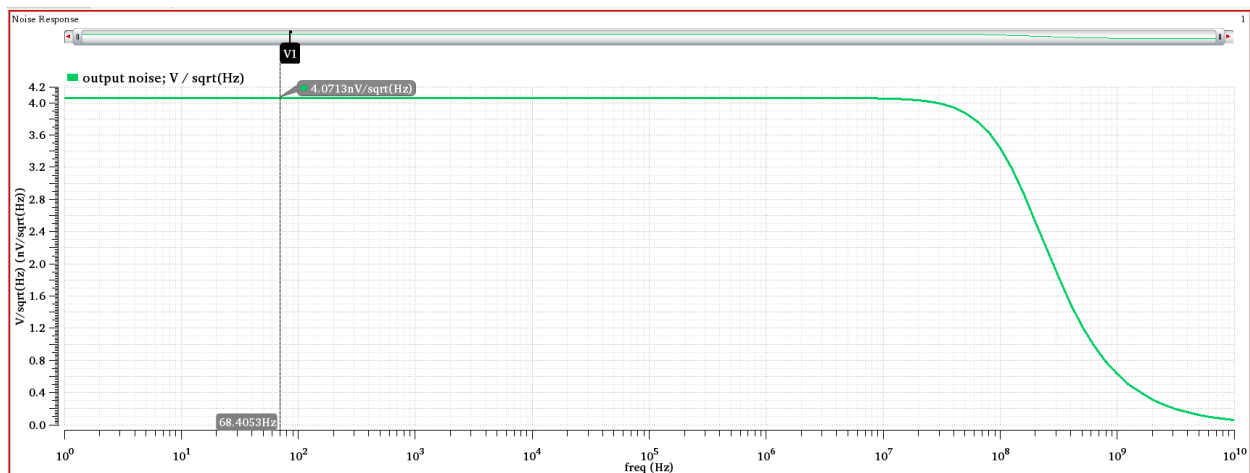
## Output noise vs frequency with the noise density annotated


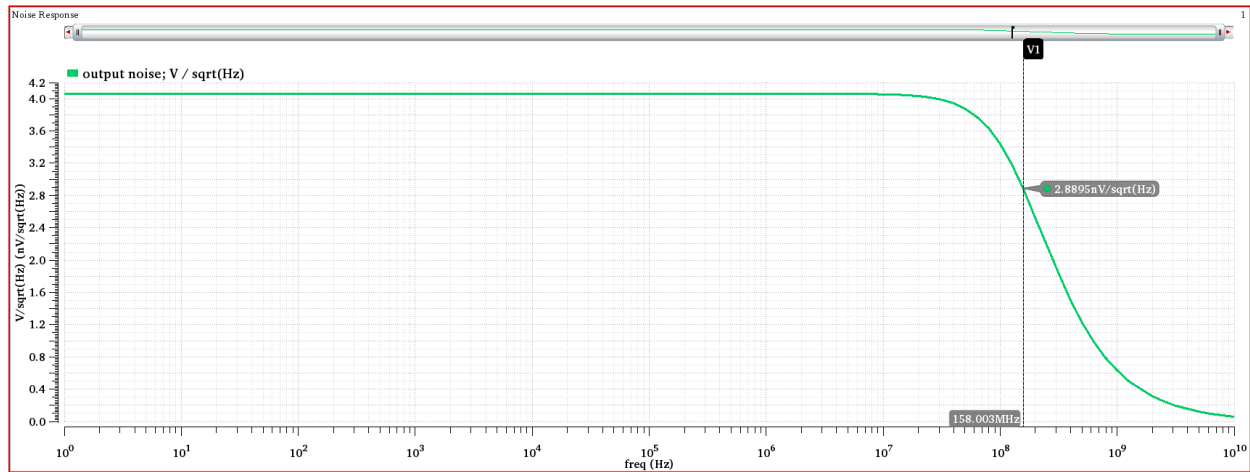
## Output noise vs frequency with the bandwidth annotated



## rms output noise

/R0	rn	4.07133e-09	100.00
/R0	fn	0	0.00

Spot Noise Summary (in V/sqrt(Hz)) at 1K Hz Sorted By Noise Contributors  
 Total Summarized Noise = 4.07133e-09  
 Total Input Referred Noise = 4.07133e-09  
 The above noise summary info is for noise data with RPAR = 1000.0

Device	Param	Noise Contribution	% Of Total
/R0	rn	6.43237e-05	100.00
/R0	fn	0	0.00

Integrated Noise Summary (in V) Sorted By Noise Contributors  
 Total Summarized Noise = 6.43237e-05  
 Total Input Referred Noise = 0.000407133  
 The above noise summary info is for noise data with RPAR = 1000.0

## Hand analysis

- Noise density

$$\text{Noise density} = \sqrt{4KTR}$$

$$\text{Noise density} = 4nV/Hz^{\frac{1}{2}}$$

- Bandwidth


$$Bandwidth = \frac{1}{2\pi RC}$$

$$Bandwidth = 159.154MHz$$

- $RMS = \sqrt{\frac{KT}{C}}$

$$RMS = 64.35\mu V$$

## Parametric sweep

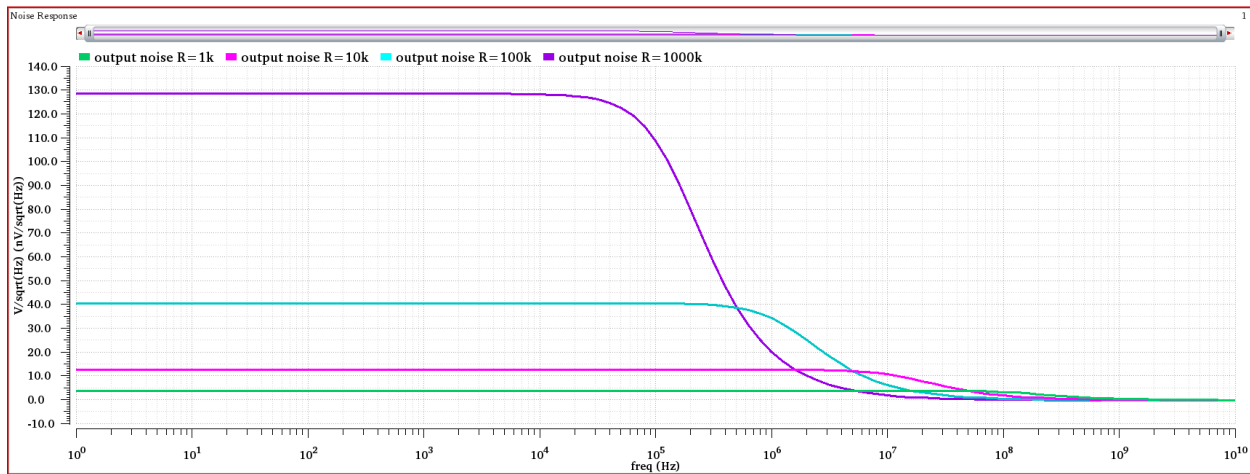

Point	Test	Output	Nominal	Spec	Weight	Pass/Fail
Parameters: RPAR=1k						
1	ITI:LAB10:1	VOUT				
1	ITI:LAB10:1	Bandwidth	158.8M			
1	ITI:LAB10:1	noise	64.32u			
Parameters: RPAR=10k						
2	ITI:LAB10:1	VOUT				
2	ITI:LAB10:1	Bandwidth	15.88M			
2	ITI:LAB10:1	noise	64.62u			
Parameters: RPAR=100k						
3	ITI:LAB10:1	VOUT				
3	ITI:LAB10:1	Bandwidth	1.588M			
3	ITI:LAB10:1	noise	64.65u			
Parameters: RPAR=1M						
4	ITI:LAB10:1	VOUT				
4	ITI:LAB10:1	Bandwidth	158.8k			
4	ITI:LAB10:1	noise	64.66u			


Comment:

When sweeping the resistor value R, the total integrated output noise remains nearly constant. This is because two opposing effects cancel each other

$$\text{Thermal noise} = 4KTR, \text{ Bandwidth} = \frac{1}{2\pi RC}$$

$$\text{And the noise} = \text{Thermal noise} \times \text{Bandwidth}$$

PART 2: LPF Transient Noise Analysis

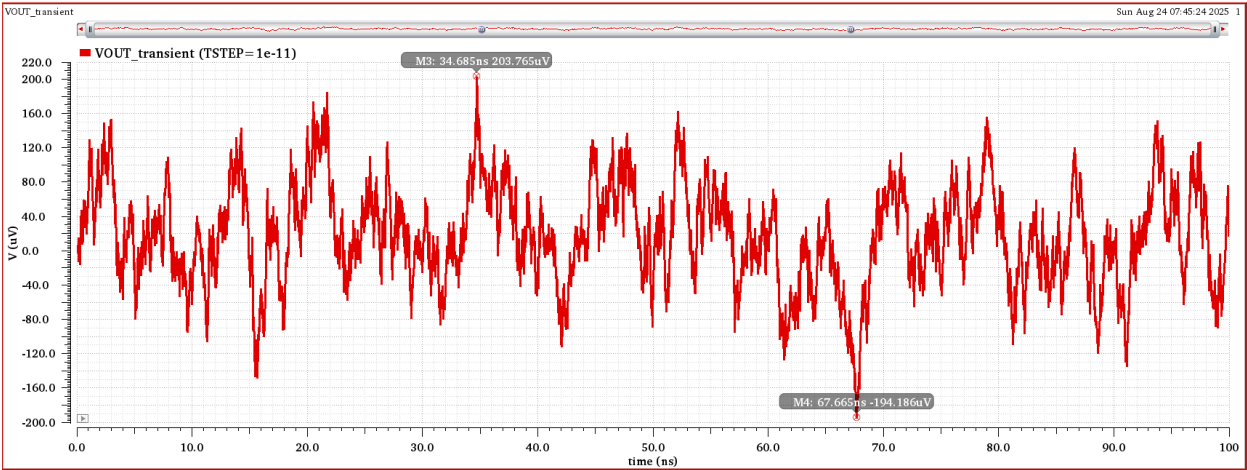

Test	Output	Nominal	Spec	Weight	Pass/Fail
ITI:LAB10:1	rms(VT("/VOUT"))	60.88u			

Comment:



The value of the output noise is smaller than the obtained value from part1

Test	Output	Nominal	Spec	Weight	Pass/Fail
ITI:LAB10:1	VOUT_transient				
ITI:LAB10:1	rms(VT("/VOUT"))	61.59u			

Comment:

Since  $T_{step}$  changed from  $\frac{TAU}{100}$  to  $\frac{TAU}{10}$  the time increased so the frequency decreases and the  $rms \propto \sqrt{f}$

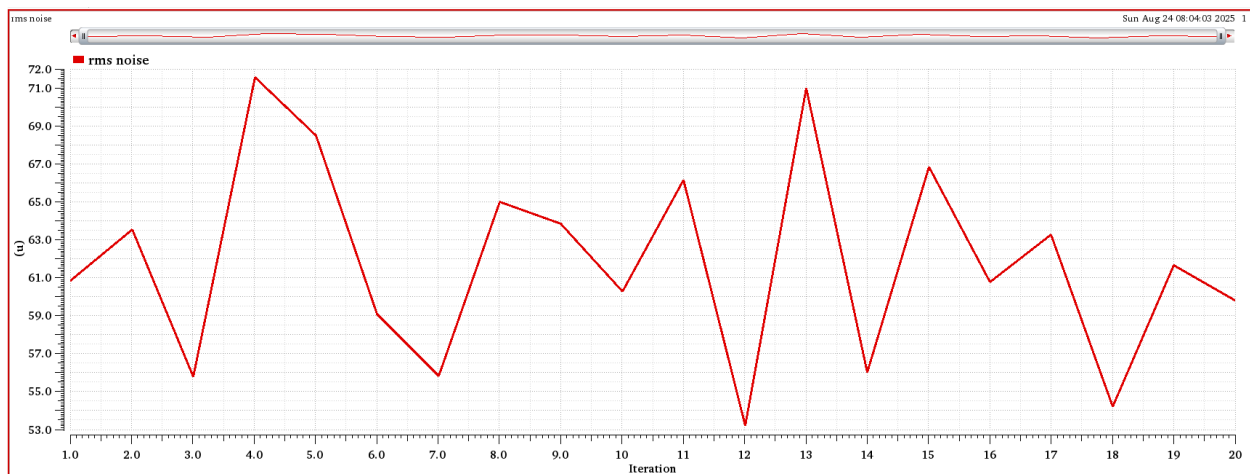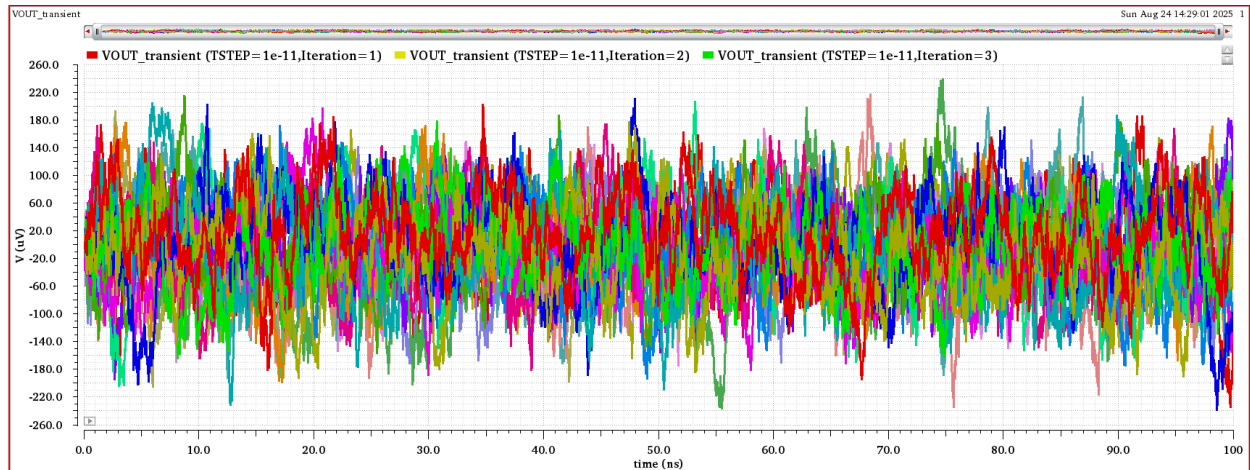
So the value of the of the rms should decrease




Test	Output	Nominal	Spec	Weight	Pass/Fail
ITI:LAB10:1	VOUT_transient				
ITI:LAB10:1	rms noise				
ITI:LAB10:1	average rms noise.	61.97u			

Current value	Part2 value	Part1 value
61.97u	61.59u	64.32u


## PART 3: 5T OTA AC Noise Analysis

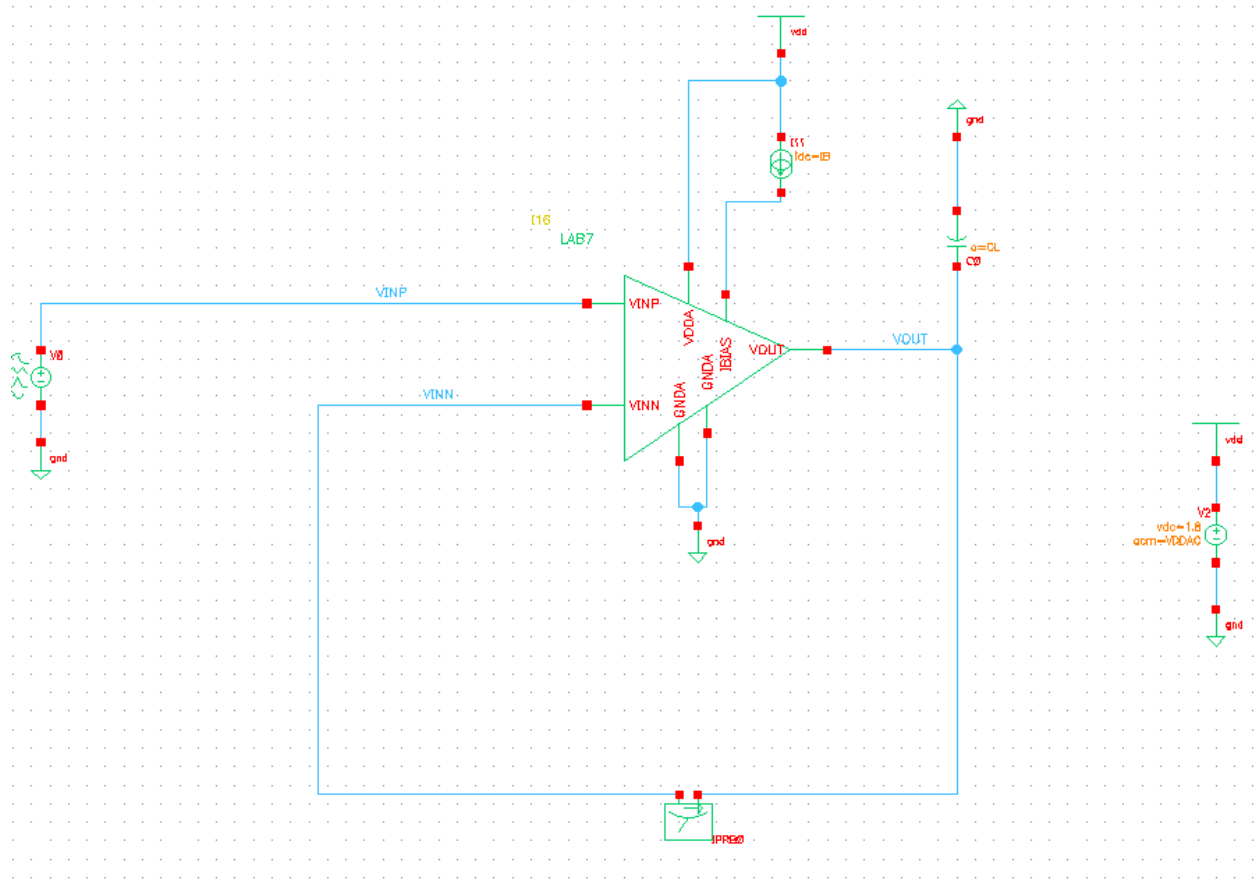


## Thermal noise

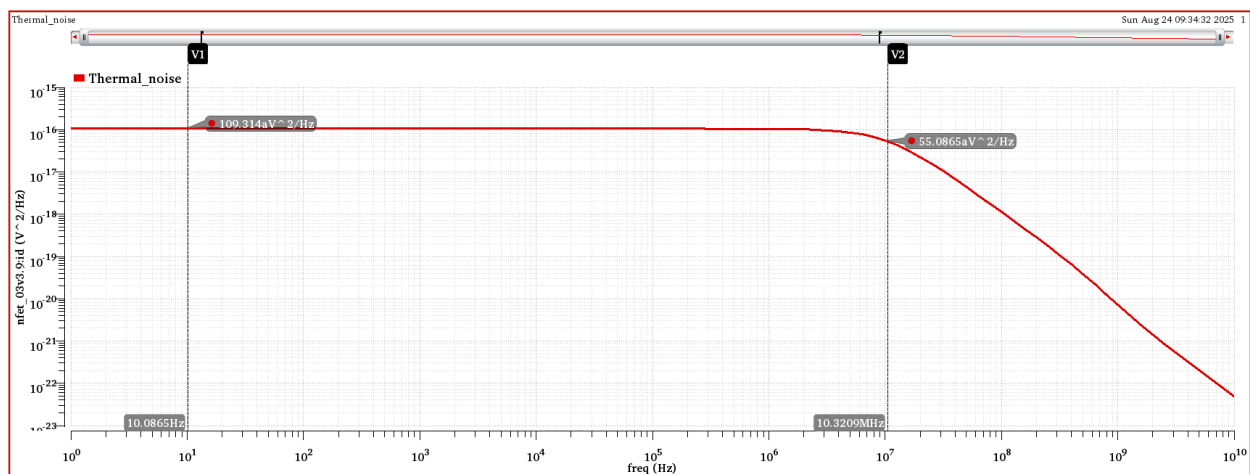



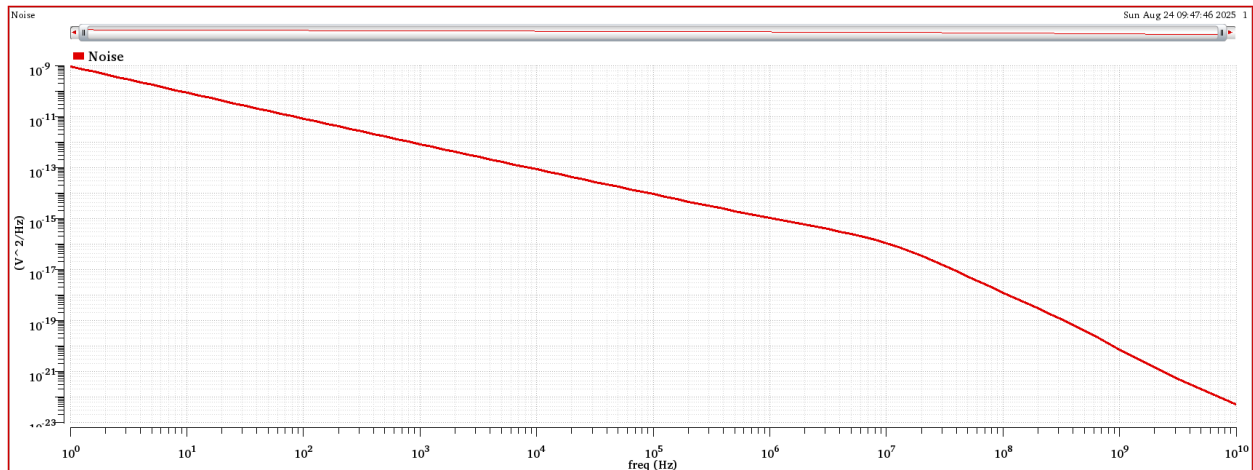

## Corner frequency

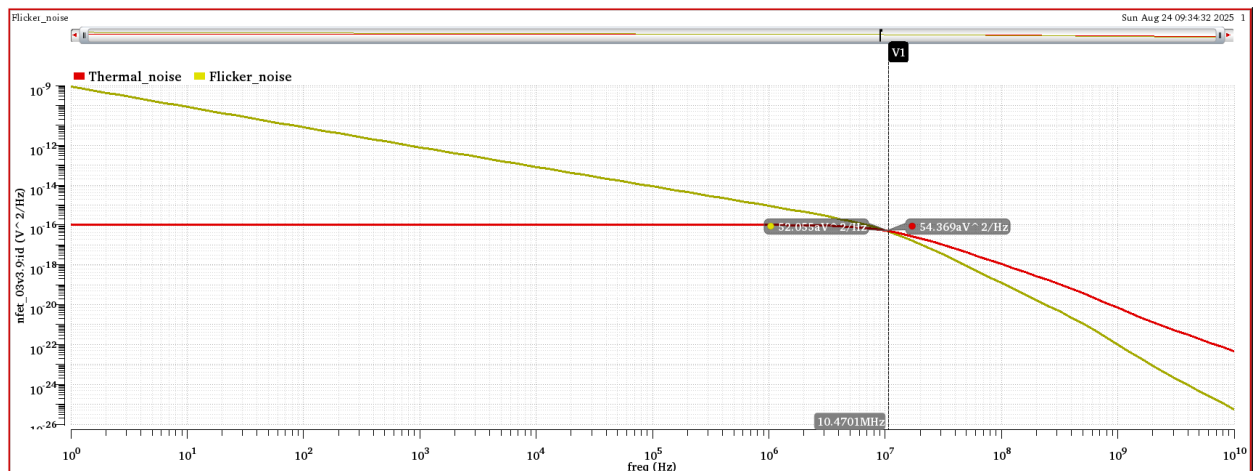

## Rms noise (due to the thermal noise only)

ITI:LAB10_OTA_part:1	rms noise	42.25u			
----------------------	-----------	--------	--	--	--

## Hand analysis

- BW

$$BW = GBW$$

$$GBW = \frac{g_{m_n}}{2\pi C_L}$$

And from LAB7

$$g_{m_n} = 0.0003283\Omega^{-1}$$

$$g_{m_p} = 0.0001964\Omega^{-1}$$

$$C_L = 5pF$$

$$BW = 10.45MHz$$

- RMS


$$V_{noise}^2 = \frac{8KT\gamma}{g_{m_n}} \left(1 + \frac{g_{m_p}}{g_{m_n}}\right)$$

$$V_{noise}^2 = 108.517 \text{ aV}^2/Hz$$



$$RMS = \sqrt{V_{noise}^2 \times BW \times \frac{\pi}{2}}$$

$$RMS = 41.28\mu V$$



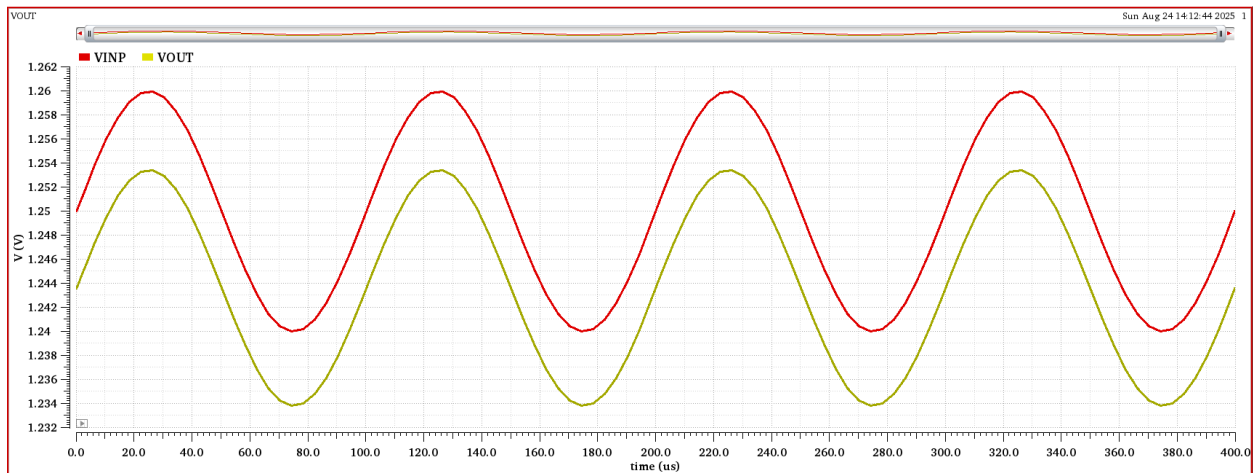
## PART 4: 5T OTA Transient Noise Analysis




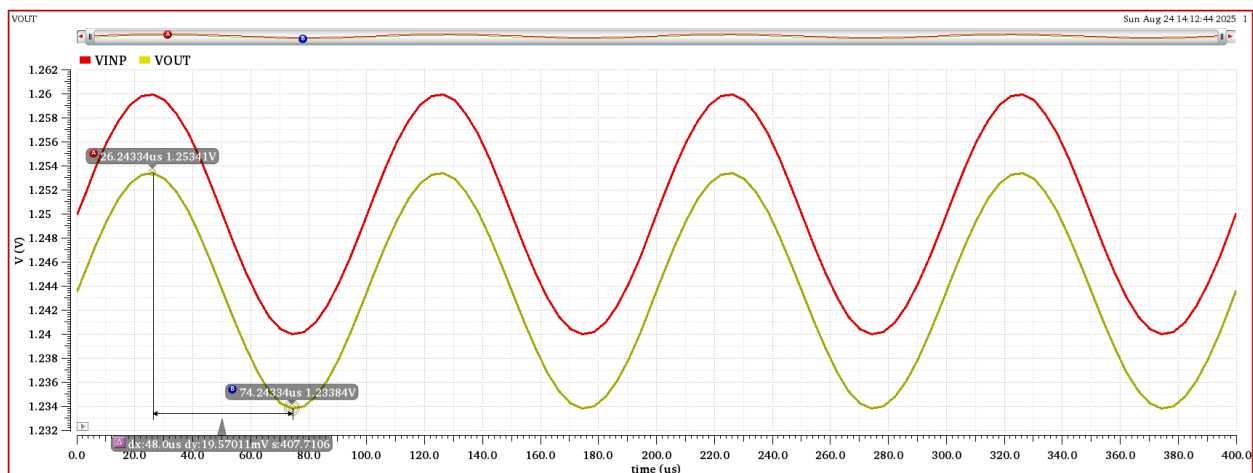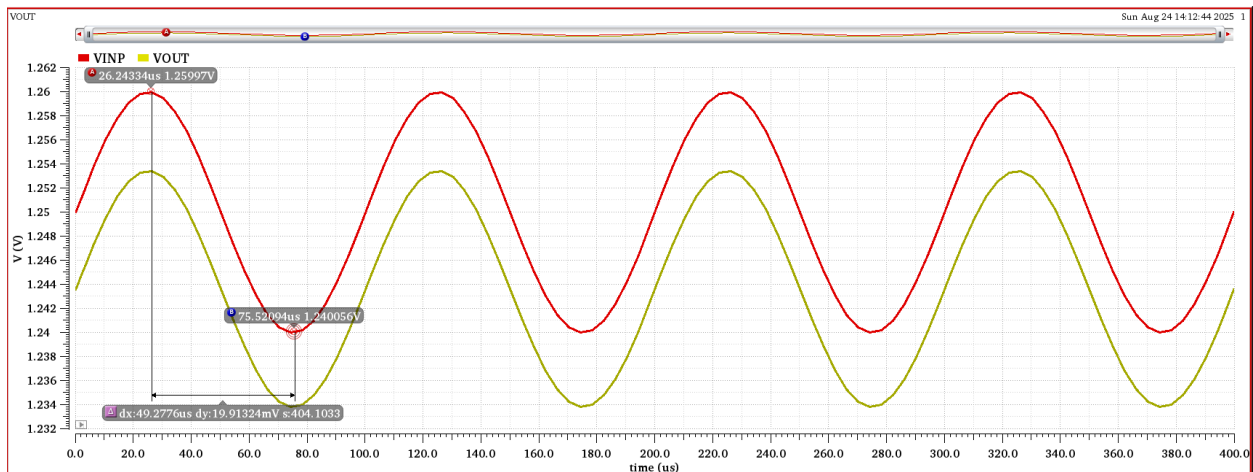Verifying if the circuit behave as a buffer



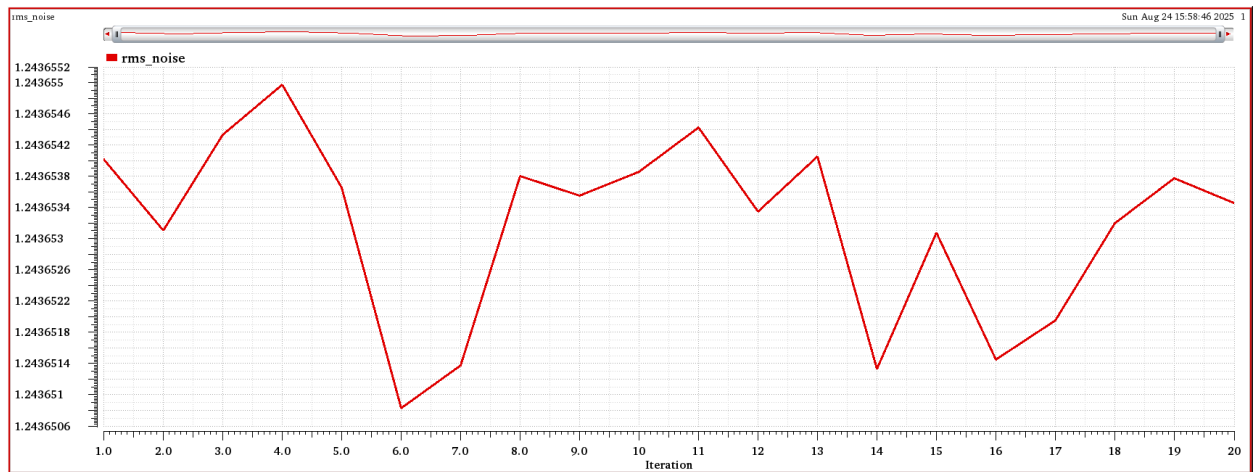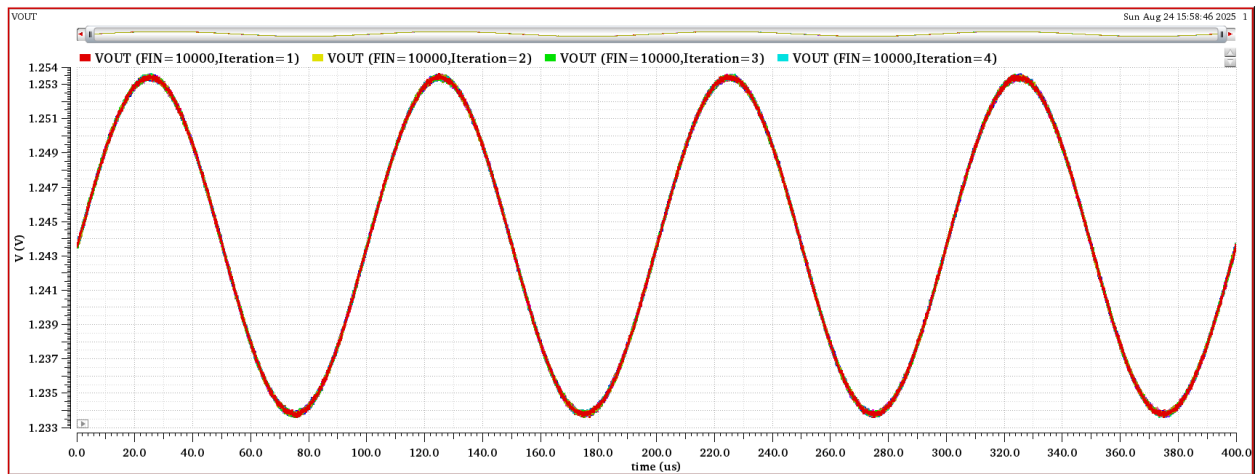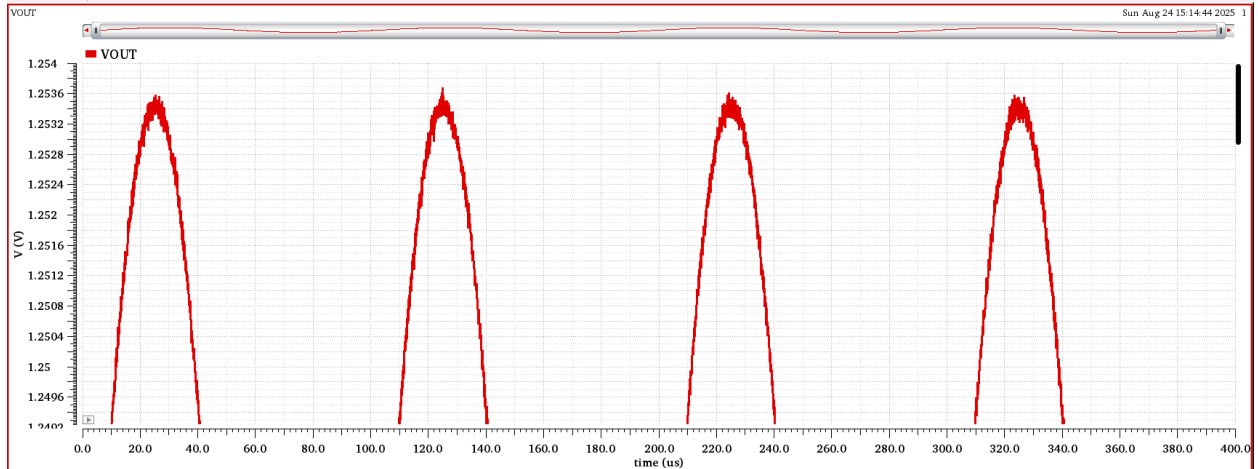Since both signals have the same peak to peak value, then this circuit behave as a buffer



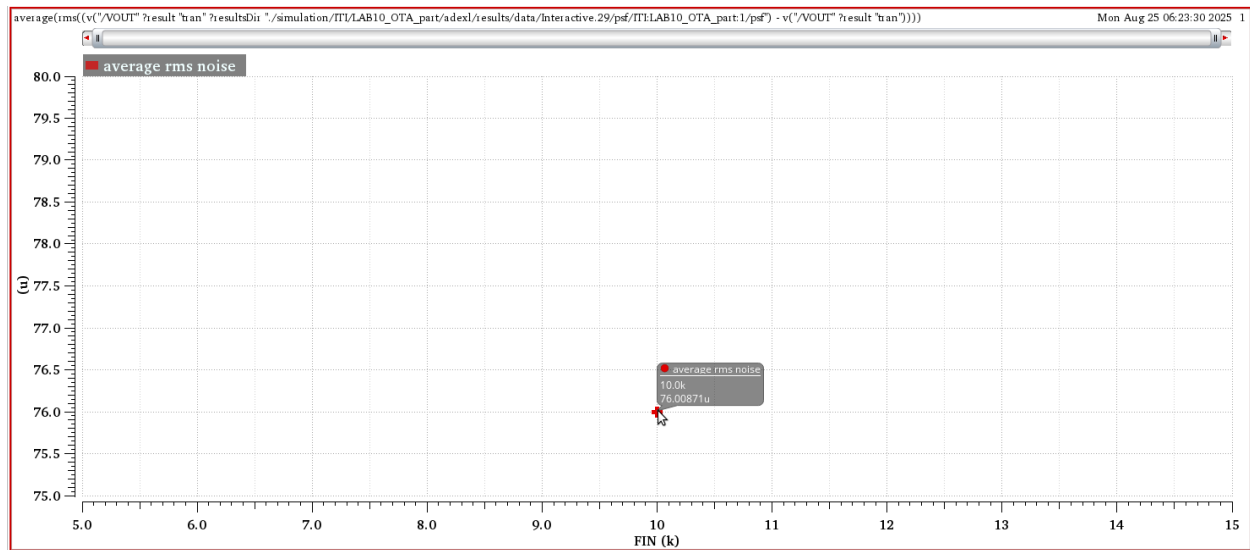

<i>average RMS from part3</i>	<i>average RMS noise from part4</i>
-----------------------------------	---

42.25u

76u