

ITI
LAB2
Common Source Amplifier

Contents

Part1: Sizing Chart.....	2
Vstar and Vov overlaid(at $V_{gsQ} = 0.816V$).....	3
IDx	3
gm_x	4
gds_x	4
Cross-Multiplication	4
A_v	5
Sizing chart	5
PART 2: CS Amplifier Schematic.....	7
DC-operating point	7
Comparing r_o and RD	8
Intrinsic gain	8
Gain vs frequency	9
Schematic.....	10
Gain Non-Linearity (Transient Analysis)	12
Is this amplifier Linear.....	13
Gain Linearization (Negative Feedback)	14
Schematic.....	14
ADT results.....	15
gm vs time.....	17


Part1: Sizing Chart

Since that the requirements is to make the gain=-10 and the gain for the common source amplifier $\approx -g_m R_d$ which could be written as $\frac{g_m}{I_D} \times R_d I_D$ and $R_d I_D = V_{Rd}$ which was given to be $1V$ $V^* = 0.25V$

$$I_D = 10 \mu A$$


$$R_D \times I_D = 1V$$

$$R_D = 100 K\Omega$$

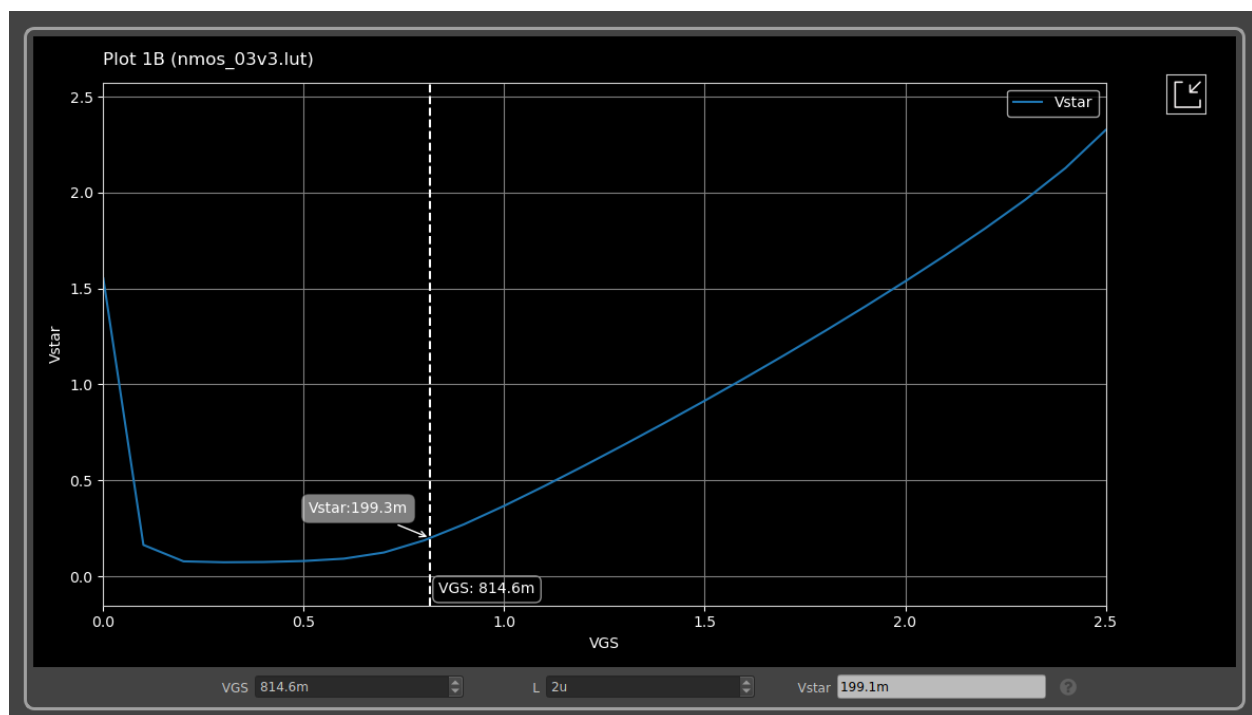


And from the graph we were able to find the value of $V_{gsQ} = 0.8146V$

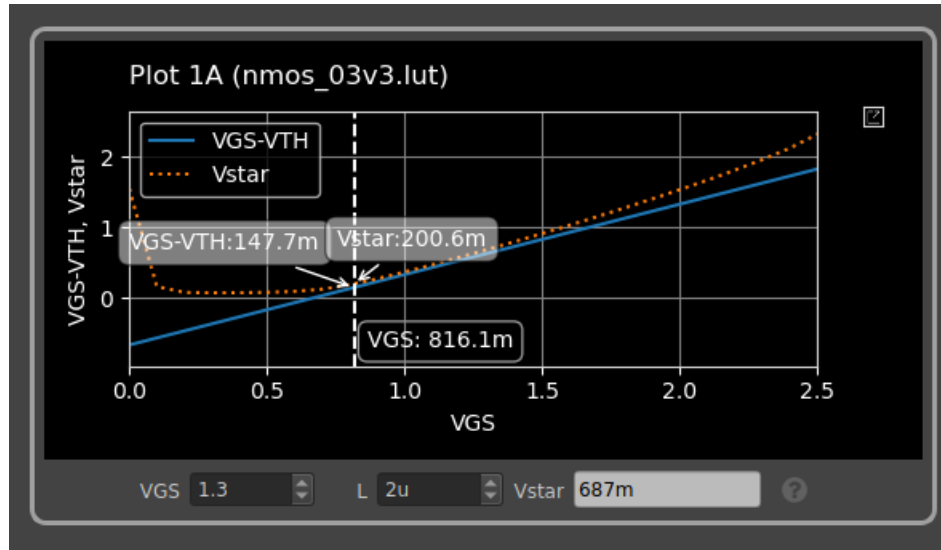Vstar and Vov overlaid(at $V_{gsQ} = 0.816V$)




And from this graph the value of $V_{ovQ} = 147.7\text{ mV}$


I_{Dx}

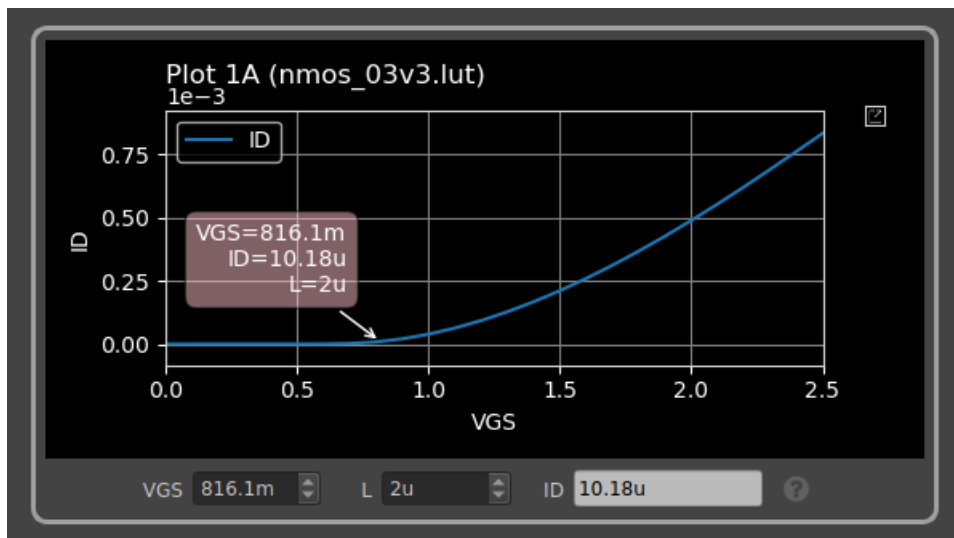

g_{mx}

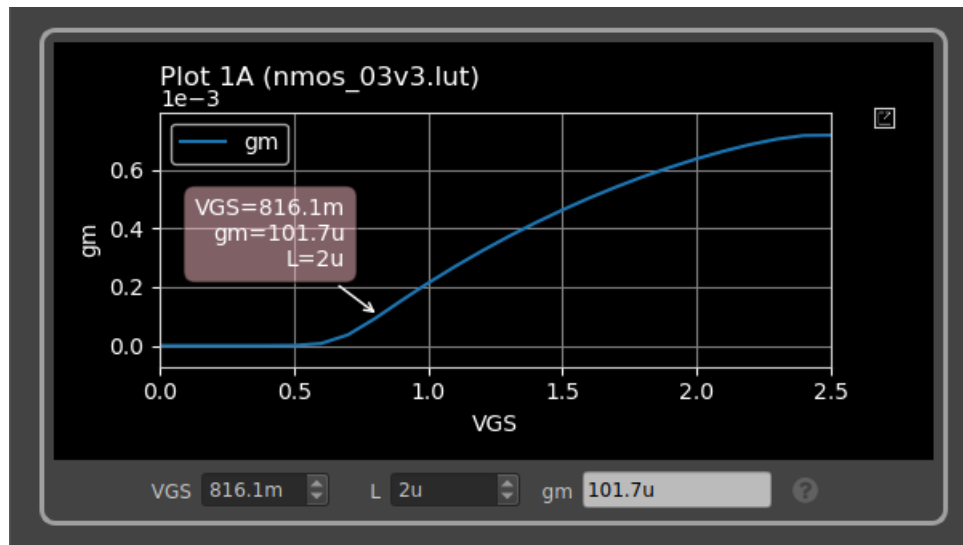

g_{dsx}

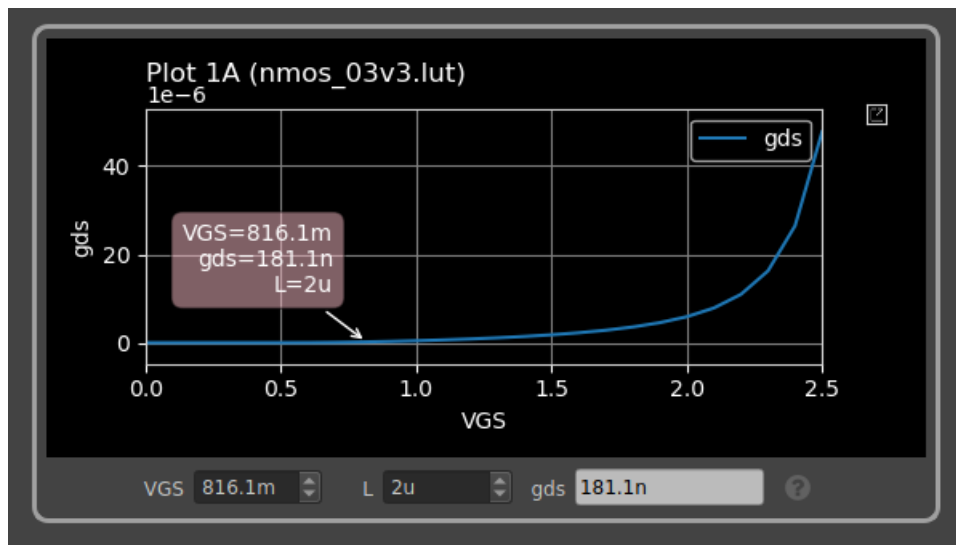

Cross-Multiplication

Now we will obtain the value of W , g_{mQ} and g_{dsQ} using $W=10\mu m$, g_{mx} and g_{dsx} and I_{Dx}

$$10\mu m \rightarrow 10.18 \mu A$$

$$W \rightarrow 10\mu A$$

Then $W=9.82\mu m$

Now we will use the same concept to find the value of g_{mQ} and g_{dsQ}

$$g_{mx} = 101.7\mu S, g_{dsx} = 181.2nS$$

$$101.7\mu S \rightarrow 10.18 \mu A$$

$$g_{mQ} \rightarrow 10\mu A$$

$$g_{mQ} \approx 100 \mu S$$

$$181.2nS \rightarrow 10.18 \mu A$$

$$g_{mQ} \rightarrow 10\mu A$$

$$g_{dsQ} = 178 nS$$

$$A_v$$

Now we will calculate the gain analytically to check if it meets the required gain

$$A_v = -g_m (r_o // R_d)$$

$$r_o = \frac{1}{g_{ds}}$$

$$A_v = -9.825$$

Sizing chart

► LUT Settings

ID ?

Vstar ?

L ?

VDS ?

VSB ?

Stack ?

Results:


	Name	TT-27.0
1	ID	10u
2	IG	N/A
3	L	2u
4	W	9.76u
5	VGS	818.1m
6	VDS	1.5
7	VSB	0
8	gm/ID	9.917
9	Vstar	201.7m
10	fT	282MEG
11	gm/gds	561.2

Y-Expr ?

▼

Parameter	Size(from graphs and cross-multiplications)
W	10 μ m
L	2 μ m
V_{gs}	816.1mV
I_D	10.18 μ A
g_m	100 μ S
g_{ds}	178 nS
V^*	200 mV
V_{ov}	147.7 mV

PART 2: CS Amplifier Schematic

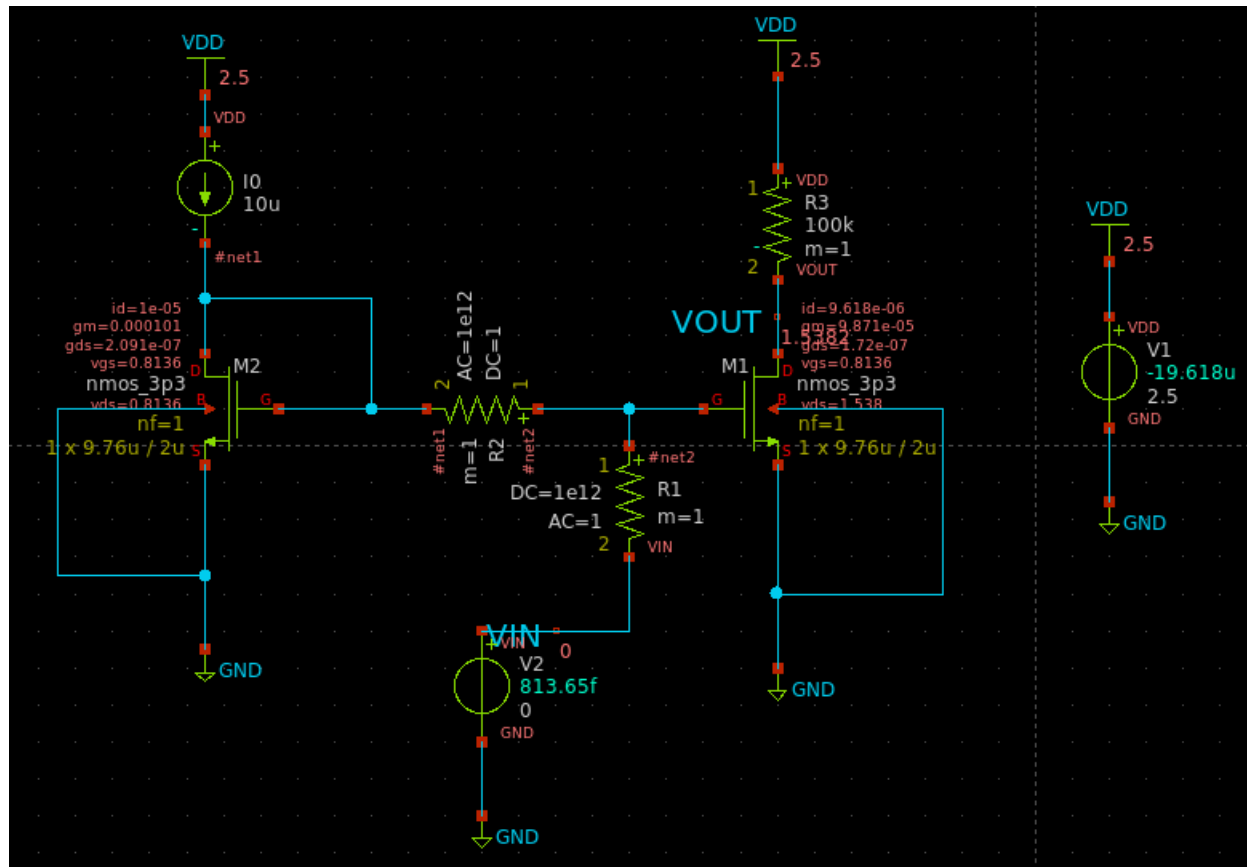

DC-operating point

Parameter	Obtained value from part1	Obtained value from part2
I_D	10 μA	9.618 μA
g_m	99.17 μS	98.71. mS
g_{ds}	176.7 nS	172 nS

As the table shows all the parameters match the obtained results with a maximum error of 2.6%

Comparing r_o and R_D

The value of $r_o = 5.66 \text{ M}\Omega$ and $R_D = 100 \text{ K}\Omega$

Meaning $r_o \approx 56.6 R_D$

If we lower the value of L the channel length effect starts to appear more which will lead to decreasing the value of r_o making it comparable to R_D

Intrinsic gain

The intrinsic gain of this circuit is 570 which is calculated using the equation

$@m.xm1.m0[gm] / @m.xm1.m0[gds]$

```
No. of Data Rows : 1
intrinsic_gain_m1 = 5.699197e+02
```

calculating the intrinsic gain analytically

$A_v = g_m r_o$, $g_m = 99.17 \mu\text{S}$ and $r_o = 5.66 \text{ M}\Omega$

$A_v(\text{intrinsic}) = 561.3$

calculating the gain analytically


$A_v = g_m (r_o // R_D)$, $g_m = 99.17 \mu\text{S}$ and $r_o = 5.66 \text{ M}\Omega$ and $R_D = 100 \text{ K}\Omega$

$A_v = 99.17(5.66 // 0.1)$

$A_v \approx 9.75$

Which means $A_v(\text{intrinsic}) \gg A_v$


Gain vs frequency

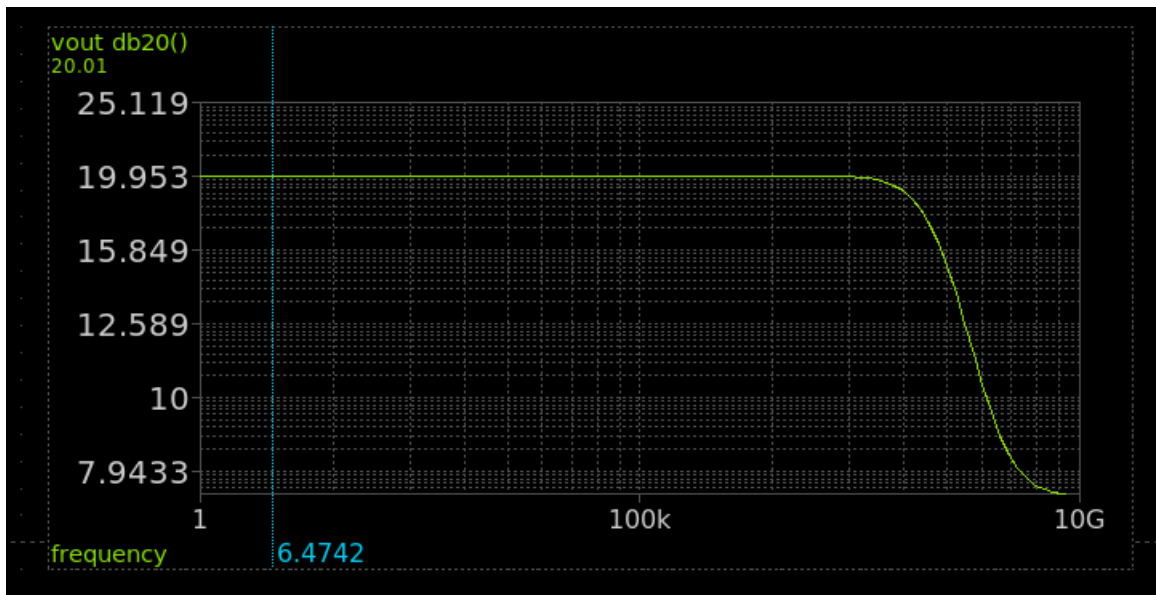


Comment: The gain vs. frequency plot shows that the amplifier maintains a nearly constant gain over a wide range of low frequencies, indicating good small-signal linearity in that region. However, at the -3 dB frequency the gain starts to drop significantly. This marks the beginning of the amplifier's high-frequency roll-off, primarily due to internal capacitances and the limited speed of the MOSFET. Beyond this point, the amplifier is no longer effective at amplifying signals without distortion or attenuation.

Gain Non-Linearity (Large Signal Operation DC Sweep)

Schematic

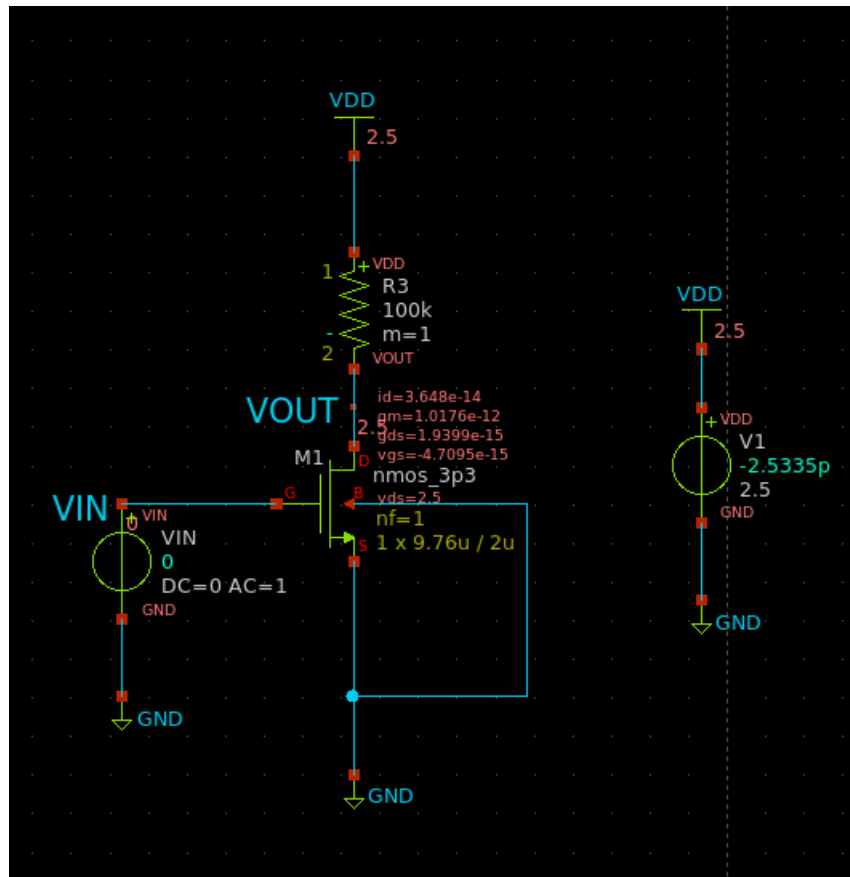

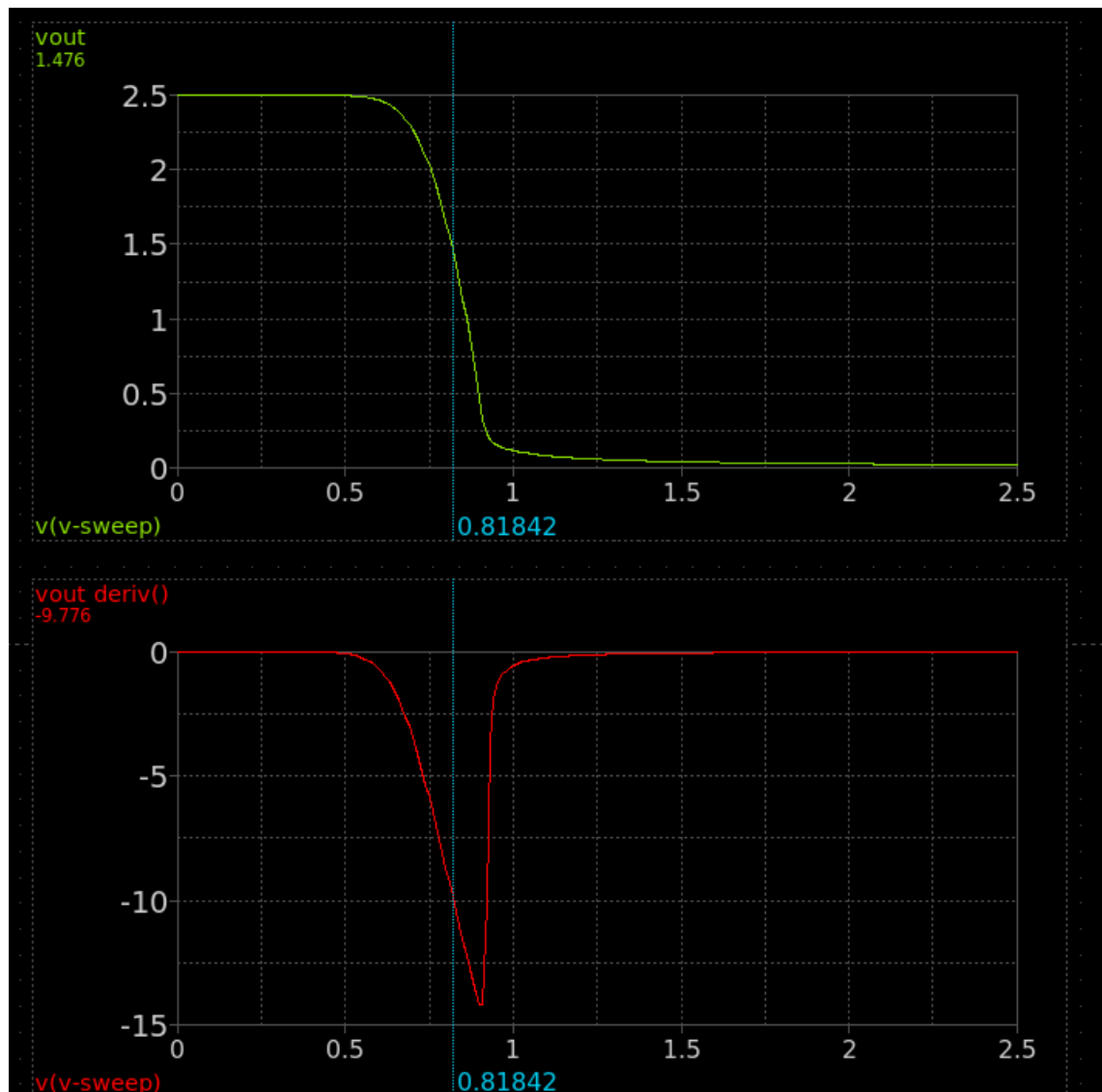

Comment:

1. The V_{OUT} vs. V_{IN} plot shows a nonlinear relationship. Initially, as V_{in} increases, V_{out} decreases gradually, but after a certain threshold, the output drops rapidly. This nonlinearity occurs because the MOSFET transitions through different regions of operation — from cutoff to saturation, and eventually to triode. In the saturation region, small changes in V_{in} cause large changes in V_{out} , which results in the steep slope. Thus, the amplifier operates linearly only over a small range of input voltages near the Q-point; outside this range, the behavior is strongly nonlinear due to the MOSFET's inherent characteristics.
2. The derivative of V_{out} with respect to V_{in} was calculated using the Cadence Calculator, and the resulting plot of derivative of V_{out} vs. V_{in} represents the small-signal gain of the


amplifier. The plot shows that the gain is not constant across all input voltages — it is high only within a narrow region around the chosen bias (Q-point), and drops off sharply outside that range.


This behavior confirms that the amplifier is only linear in a small region near the Q-point. In this region, the transistor operates in saturation, where g_m is relatively stable, resulting in a well-defined and predictable gain. However, as V_{IN} moves away from the Q-point:

- At low V_{IN} the MOSFET enters cutoff, causing gain to approach zero.
- At high V_{IN} , the device moves into the triode region, also degrading the gain.

Thus, the gain is not independent of the input; it varies strongly with V_{IN} except near the Q-point. This emphasizes the importance of carefully biasing the MOSFET to ensure linear operation in analog amplifier design.

Gain Non-Linearity (Transient Analysis)

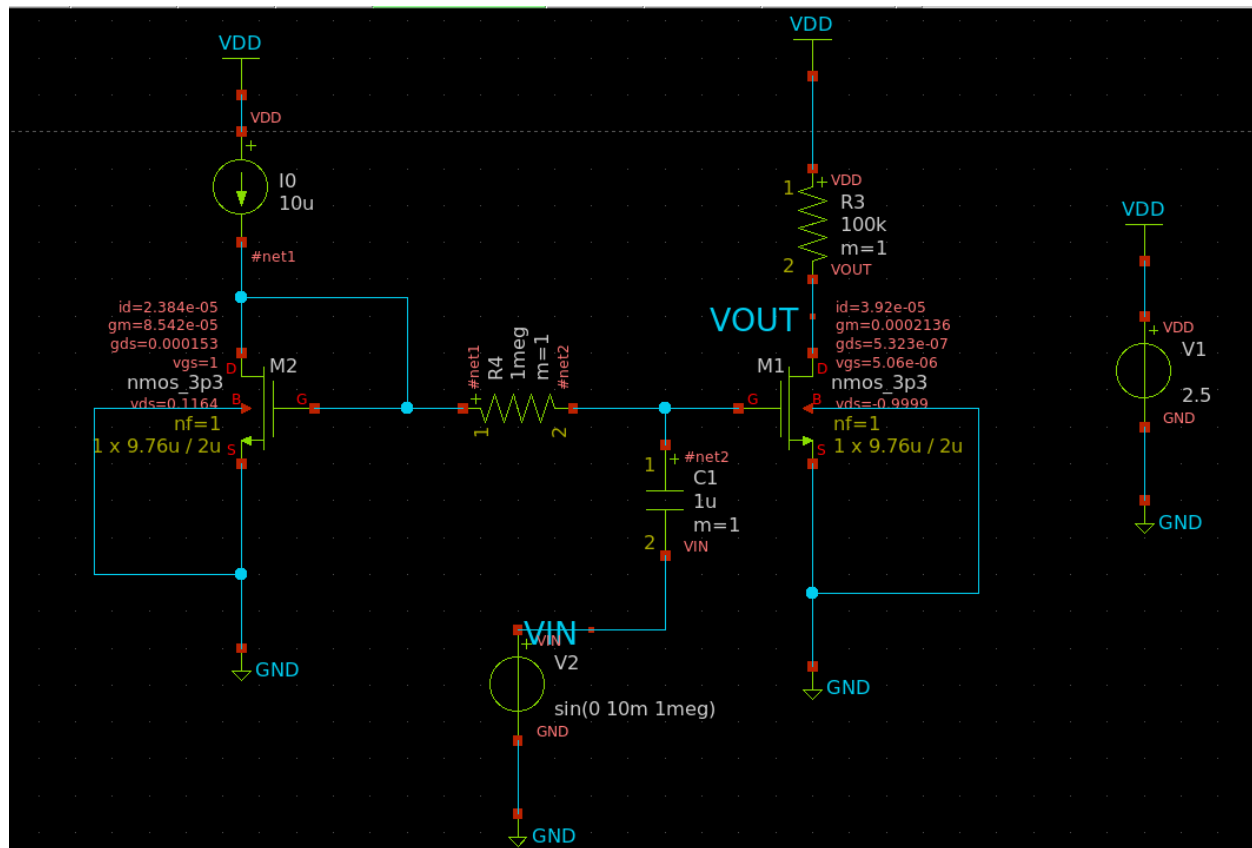

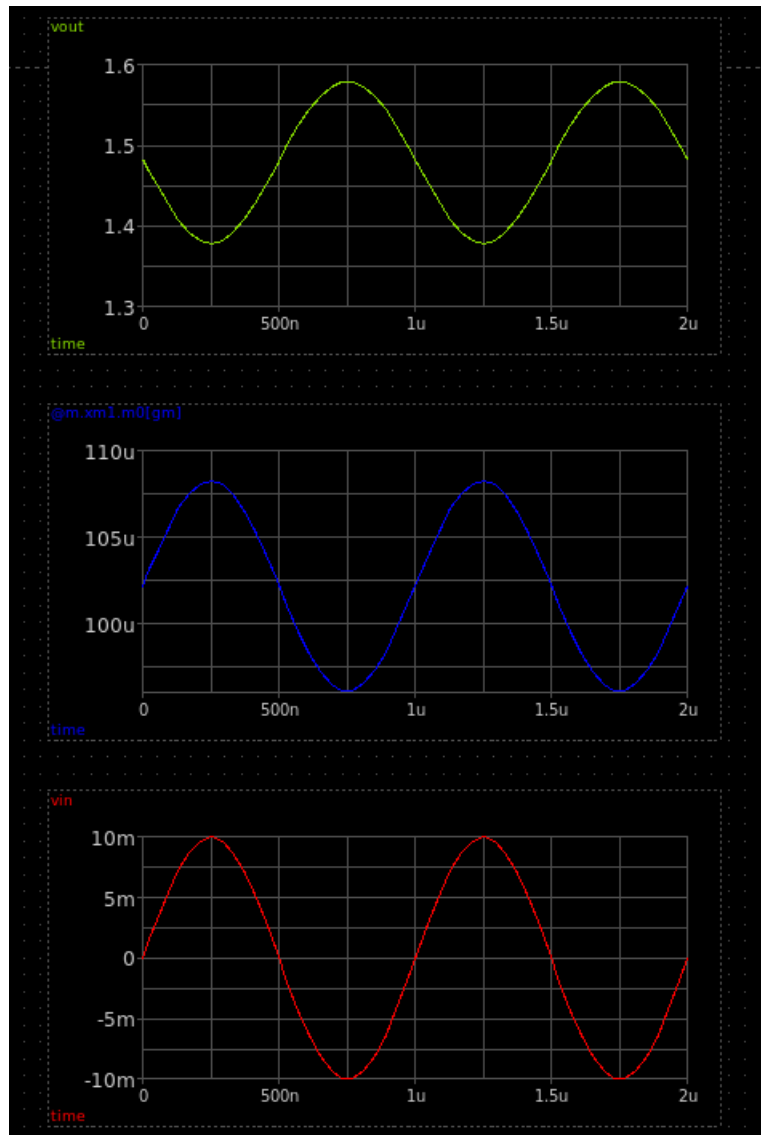

Comment:


g_m varies with the input signal because it depends on V_{gs} , which changes as the input changes. This means the gain of the amplifier also varies, leading to nonlinear distortion if the input signal is too large. For accurate small-signal operation, the input should be limited to a range where g_m can be considered approximately constant around the Q-point.

Is this amplifier Linear

This amplifier is nonlinear as from the transient simulation, the g_m vs time plot shows a sinusoidal variation, this indicates that the circuit is nonlinear, since in a linear amplifier, g_m should remain constant. The observed g_m fluctuation confirms the dependency of transconductance on the input signal amplitude, which is a typical characteristic of MOSFET-based amplifiers in large-signal conditions.

Gain Linearization (Negative Feedback)

Schematic

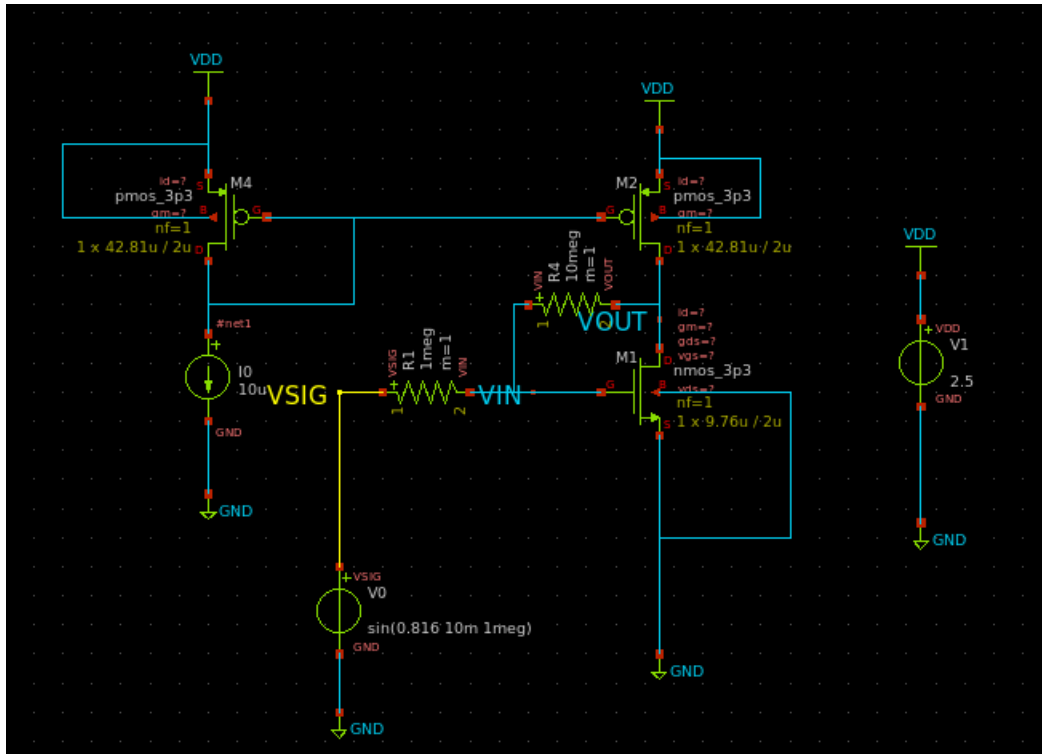

$$R_{in} = \frac{R_F}{A_v}$$

Then $R_{in} = 1M\Omega$

ADT results

▼ LUT Settings

LUT ?

Corner All ?

Temp (°C) All ?

Frequency ?

ID ?

Vstar ?

L ?

VDS ?

VSB ?


Stack ?

Results:

	Name	TT-27.0
3	L	2u
4	W	42.81u
5	VGS	936.8m
6	VDS	1


Y-Expr ?

▼

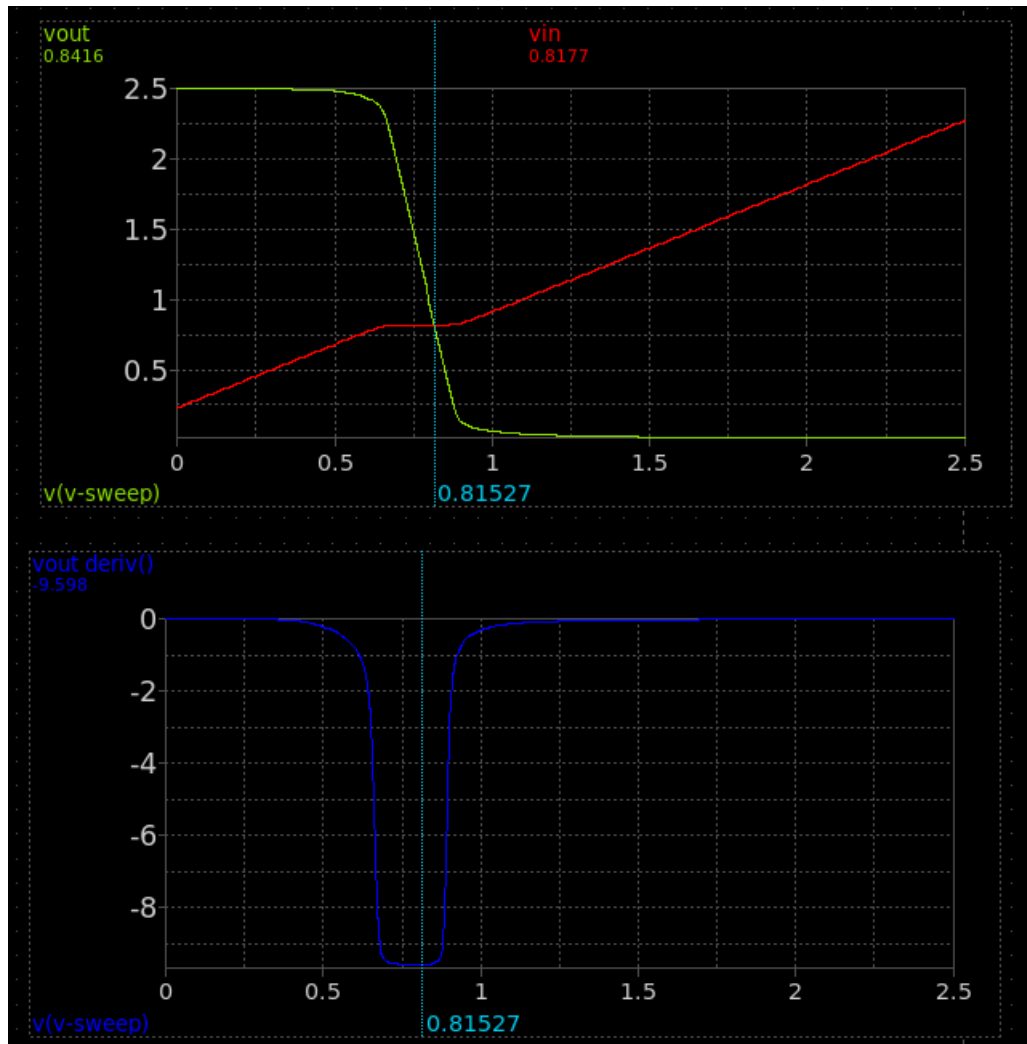

Comment: The curves of V_{IN} and V_{OUT} cross at the point where the input signal equals the quiescent gate voltage of M1. At this point, $V_{OUT} = V_{IN}$, and no current flows in the feedback resistors. This point represents the bias point of the amplifier, where the system is balanced, and the MOSFET operates at its designed operating point (V_{gsQ})

g_m vs time

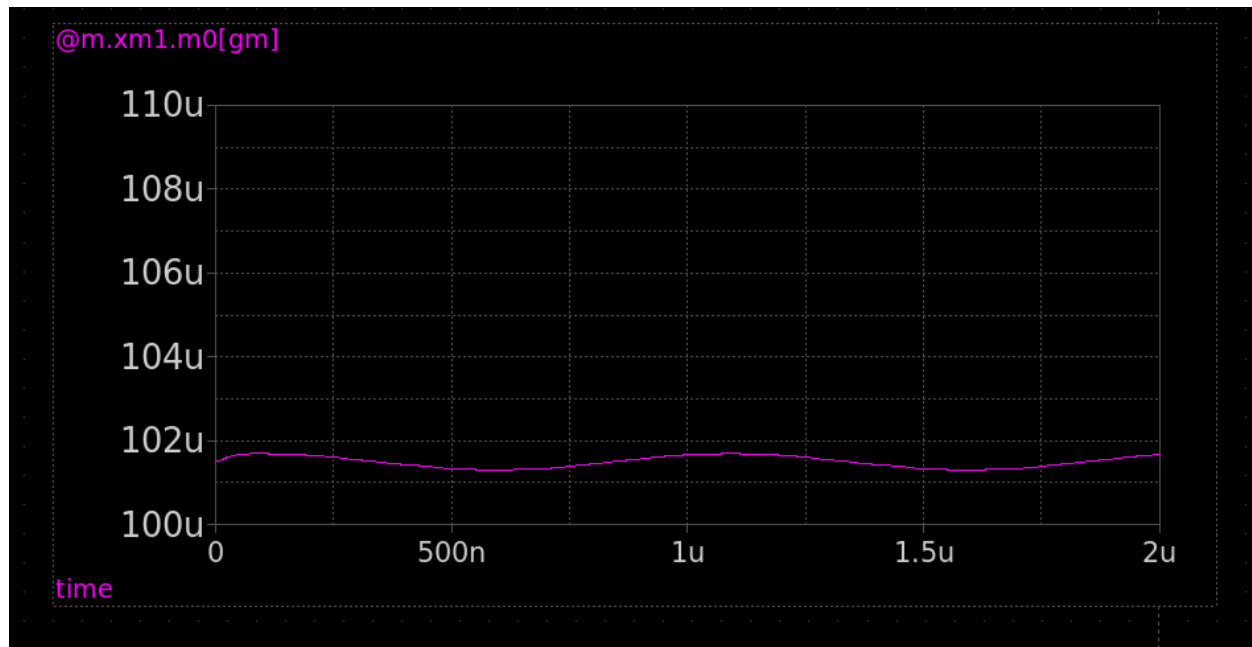

Comment: By running the transient simulation, the g_m vs time plot for the feedback amplifier shows that the g_m matches exactly the g_m of the resistive-loaded open-loop amplifier, confirming that both circuits operate at the same quiescent transconductance. However, the variation of g_m over time is significantly lower in the feedback circuit due to the stabilizing effect of negative feedback. This reduced g_m fluctuation indicates improved linearity, as the feedback minimizes the impact of input signal changes on the transistor's operating point, keeping g_m more constant compared to the open-loop case.